

920M CONTROL DECK seen from wiring side

H66: 5 8 7 RxInt3, Rx----	G66: 5 8 7 RxRIP, RxROP	F66: 5 7 3 TxA02, TxAP3	E66: 5 7 3 TxD08, TxDP8
H65: 5 8 7 RxInt1, RxInt2	G65: 5 7 3 TxSOP, TxSIP	F65: 5 7 3 TxA07, TxA08	E65: 5 7 3 TxD05, TxDP5
H64: 5 6 7 Nand+5*inv	G64: 5 6 2 4*2Nand	F64: 5 7 3 TxA06, TxA05	E64: 5 7 3 TxD15, TxD16
H63: 5 6 7 Nand+5*inv	G63: 5 6 2 4*2Nand	F63: 5 7 3 TxD07, TxDP7	E63: 5 7 3 TxD17, TxD18
H62: 5 6 7 Nand+5*inv	G62: 5 6 4 2*4Nand	F62: 5 7 3 TxA01, TxAP1	E62: 5 7 3 TxD01, TxDP1
H61: 5 6 4 2*4Nand	G61: 5 6 2 4*2Nand	F61: 5 7 3 TxD13, TxD14	E61: 5 7 3 TxD06, TxDP6
H60: 5 6 4 2*4Nand	G60: 5 6 4 2*4Nand	F60: 5 7 3 TxD12, TxD11	E60: 5 7 3 TxD02, TxDP2
H59: 5 6 4 2*4Nand	G59: 5 6 4 2*4Nand	F59: 5 7 3 TxA03, TxA04	E59: 5 7 3 TxD04, TxDP4
H58: 5 6 4 2*4Nand	G58: 5 8 7 RxRAQ, RxPAQ	F58: 5 7 3 TxD09, TxD10	E58: 5 7 3 TxD03, TxDP3
H57: 5 6 4 2*4Nand	G57: typeG?	F57: 5 7 3 TxA11, Tx----	E57: -- 0 6 cables
H56: 5 6 2 4*2Nand	G56: typeG?	F56: 5 7 3 TxA10, TxA09	E56: -- 0 5 cables
H55: 5 6 2 4*2Nand	G55: typeG?	F55: 5 7 3 TxIRset, TxXRset	E55: -- 0 4 cables
H54: 5 6 2 4*2Nand	G54: -- 7 9 6*150ohm	F54: -- 7 7 Margins	E54: -- 0 3 cables
H53: 5 5 3 Eupper, Elower	G53: 5 6 3 2*Nand+2*Buff	F53: -- 7 7 Margins	E53: -- 0 2 cables
H52: 5 6 2 4*2Nand	G52: 5 0 4 Reset & PwrGd	F52: 5 6 4 2*4Nand	E52: -- 0 1 cables

H51: 5 6 5 2*4Buff	G51: 5 6 5 2*4Buff	F51: 5 6 6 3*Expander	E51: -- 0 1 cables
H50: type76	G50: 5 6 5 2*4Buff	F50: 5 6 4 2*4Nand	E50: -- 0 3 cables
H49: type76	G49: 5 6 5 2*4Buff	F49: 5 6 3 2*Nand+2*Buff	E49: -- 0 5 cables
H48: type76	G48: 5 6 5 2*4Buff	F48: 5 6 7 Nand+5*inv	E48: -- 0 2 cables
H47: 5 6 7 Nand+5*inv	G47: 5 6 5 2*4Buff	F47: 5 6 4 2*4Nand	E47: 5 0 9 Init Instr Latch
H46: type75	G46: 5 6 4 2*4Nand	F46: 5 6 6 3*Expander	E46: 5 6 4 2*4Nand
H45: type75	G45: 5 6 4 2*4Nand	F45: 5 6 6 3*Expander	E45: 5 6 4 2*4Nand
H44: type75	G44: 5 6 2 4*2Nand	F44: 5 6 4 2*4Nand	E44: 5 6 1 4*Decoder
H43: 5 6 4 2*4Nand	G43: 5 6 3 2*Nand+2*Buff	F43: -- 7 8 6*10Kohm	E43: 5 6 4 2*4Nand
H42: 5 6 4 2*4Nand	G42: 5 6 2 4*2Nand	F42: 5 5 1 "Areg19"	E42: 5 6 4 2*4Nand
H41: 5 6 2 4*2Nand	G41: 5 6 4 2*4Nand	F41: 5 7 3 TxXTrWr, TxXlSt	E41: 5 6 2 4*2Nand
H40: 5 6 2 4*2Nand	G40: 5 6 3 2*Nand+2*Buff	F40: 5 8 7 RxXRdR, RxXWrR	E40: 5 6 4 2*4Nand
H39: 5 7 3 TxPRQ, TxRRQ	G39: 5 6 2 4*2Nand	F39: 5 7 3 TxXTrRd, TxBlock	E39: 5 6 2 4*2Nand

H32: 5 6 7 Nand+5*inv	G32: 5 6 2 4*2Nand	F32: 5 6 4 2*4Nand	E32: -- 7 8 6*10Kohm
H31: 5 6 4 2*4Nand	G31: 5 6 2 4*2Nand	F31: 5 6 4 2*4Nand	E31: 5 6 2 4*2Nand
H30: 5 5 1 Clatch6	G30: 5 6 7 Nand+5*inv	F30: 5 6 5 2*4Buff	E30: 5 6 4 2*4Nand
H29: 5 6 0 Cadder6	G29: 5 6 2 4*2Nand	F29: 5 6 6 3*Expander	E29: 5 6 4 2*4Nand
H28: 5 5 1 Clatch5	G28: 5 6 4 2*4Nand	F28: 5 6 6 3*Expander	E28: 5 0 2 4*2Nand
H27: 5 6 0 Cadder5	G27: 5 6 1 4*Decoder	F27: 5 6 5 2*4Buff	E27: 5 6 2 4*2Nand
H26: 5 5 1 Clatch4	G26: 5 6 1 4*Decoder	F26: 5 6 6 3*Expander	E26: 5 6 3 2*Nand+2*Buff
H25: 5 6 0 Cadder4	G25: 5 6 1 4*Decoder	F25: 5 6 5 2*4Buff	E25: 5 6 3 2*Nand+2*Buff
H24: 5 6 7 Nand+5*inv	G24: 5 6 4 2*4Nand	F24: 5 6 6 3*Expander	E24: 5 6 2 4*2Nand
H23: 5 6 3 2*Nand+2*Buff	G23: 5 6 1 4*Decoder	F23: 5 6 4 2*4Nand	E23: -- 0 2 cables
H22: 5 6 4 2*4Nand	G22: 5 6 4 2*4Nand	F22: 5 6 6 3*Expander	E22: -- 0 5 cables
H21: 5 6 6 3*Expander	G21: 5 6 1 4*Decoder	F21: 5 6 4 2*4Nand	E21: -- 0 3 cables
H20: -- 7 8 6*10Kohm	G20: 5 6 4 2*4Nand	F20: 5 6 7 Nand+5*inv	E20: -- 0 1 cables

H19: 5 6 4 2*4Nand	G19: 5 6 1 4*Decoder	F19: 5 6 2 4*2Nand	E19: -- 0 1 cables
H18: 5 6 6 3*Expander	G18: 5 6 1 4*Decoder	F18: 5 6 5 2*4Buff	E18: -- 0 2 cables
H17: 5 6 3 2*Nand+2*Buff	G17: 5 6 1 4*Decoder	F17: 5 6 6 3*Expander	E17: -- 0 3 cables
H16: 5 6 4 2*4Nand	G16: 5 6 1 4*Decoder	F16: 5 6 4 2*4Nand	E16: -- 0 4 cables
H15: 5 6 2 4*2Nand	G15: 5 6 1 4*Decoder	F15: 5 6 2 4*2Nand	E15: -- 0 5 cables
H14: 5 6 1 4*Decoder	G14: 5 6 1 4*Decoder	F14: 5 6 4 2*4Nand	E14: -- 0 6 cables
H13: 5 6 2 4*2Nand	G13: 5 6 1 4*Decoder	F13: 5 6 5 2*4Buff	E13: 5 6 2 4*2Nand
H12: 5 6 1 4*Decoder	G12: 5 6 1 4*Decoder	F12: 5 6 6 3*Expander	E12: 5 6 3 2*Nand+2*Buff
H11: 5 6 7 Nand+5*inv	G11: 5 6 1 4*Decoder	F11: 5 6 5 2*4Buff	E11: 5 6 4 2*4Nand
H10: 5 6 0 Cadder3	G10: 5 6 2 4*2Nand	F10: 5 6 3 2*Nand+2*Buff	E10: 5 6 3 2*Nand+2*Buff
H09: 5 5 1 Clatch3	G09: 5 6 1 4*Decoder	F09: 5 6 3 2*Nand+2*Buff	E09: 5 6 2 4*2Nand
H08: 5 6 0 Cadder2	G08: 5 6 4 2*4Nand	F08: 5 6 5 2*4Buff	E08: 5 6 5 2*4Buff
H07: 5 5 1 Clatch2	G07: 5 6 1 4*Decoder	F07: 5 6 6 3*Expander	E07: 5 6 3 2*Nand+2*Buff
H06: 5 6 0 Cadder1	G06: 5 8 7 RxDP5, RxDP6	F06: 5 8 7 RxDP1, RxDP2	E06: 5 6 7 Nand+5*inv
H05: 5 5 1 Clatch1	G05: 5 8 7 RxDP7, RxDP8	F05: 5 8 7 RxDP3, RxDP4	E05: 5 6 7 Nand+5*inv